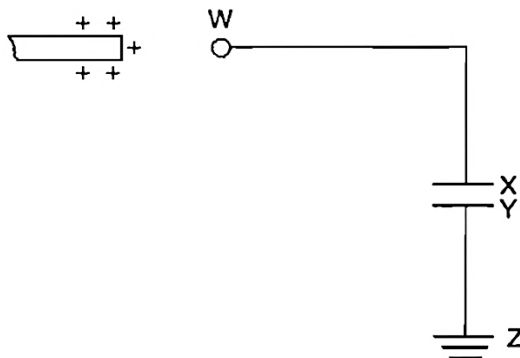


Topic 16: Capacitors

Solutions to Exercises

Exercise 1

- 1.1** An uncharged capacitor is connected between earth Z and a terminal W. A positively charged rod is brought close to W.



Which of the following describes the movement of charge?

- A** Electrons move from W to X and from Y to Z.
- B** Electrons move from W to X but not from Y to Z.
- C** Electrons move from X to W and from Z to Y.
- D** Electrons move from X to W but not from Z to Y.

Answer: C

Electrons near W attracted to positive rod causing electrons to move towards W.

X becomes net positive.

X being positive attracts electrons to move towards Y, drawing electrons from the earth.

- 1.2** A $20\ \mu\text{F}$ capacitor is charged by a constant current of $10\ \text{mA}$. If the capacitor is initially uncharged, how long does it take for the potential difference across the capacitor to reach $300\ \text{V}$?

- A** $6.0 \times 10^{-4}\ \text{s}$ **B** $0.60\ \text{s}$ **C** $15\ \text{s}$ **D** $6.0 \times 10^5\ \text{s}$

Answer: B


Charge on capacitor when p.d. is $300\ \text{V}$, $Q = CV = (20 \times 10^{-6})(300) = 0.006\ \text{C}$

Since current = charge / time,

$$10 \times 10^{-3} = 0.006 / t$$

$$t = 0.6\ \text{s}$$

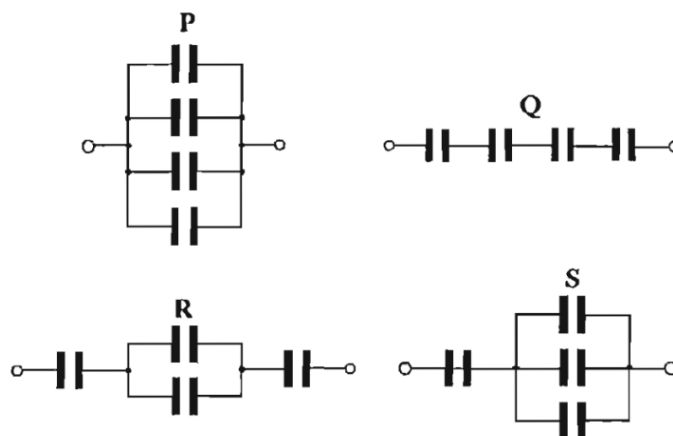1.3 Four identical capacitors are connected as shown.



Which of the following lists the arrangements in order of **decreasing** capacitance?

A PQRS

B PSRQ

C QRSP

D QSRP

Answer: B

Let C be the capacitance of each capacitor.

Circuit P: $C_{\text{total}} = C + C + C + C = 4C$


Circuit Q: $C_{\text{total}} = [1/C + 1/C + 1/C + 1/C]^{-1} = C/4$

Circuit R: $C_{\text{total}} = [1/C + 1/(C + C) + 1/C]^{-1} = 2C/5$

Circuit S: $C_{\text{total}} = [1/C + 1/(C + C + C)]^{-1} = 3C/4$

Decreasing capacitance is PSRQ.

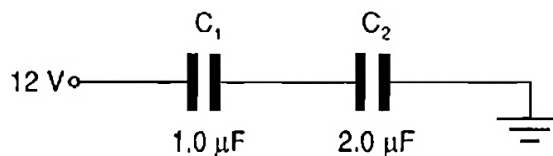1.4 Two capacitors are connected in series as shown.



What is the charge carries by each of these capacitors?

	charge on C_1 / μC	charge on C_2 / μC
A	4.0	4.0
B	4.0	8.0
C	8.0	4.0
D	8.0	8.0

Answer: D

$C_{\text{total}} = (1/1.0 + 1/2.0)^{-1} = 2/3 \mu\text{F}$


p.d. across equivalent capacitor $V = 12 - 0 = 12 \text{ V}$

Charge on equivalent capacitor = $C_{\text{total}} V = (2/3) (12) = 8 \mu\text{C}$

Capacitors in series have the same amount of charge.

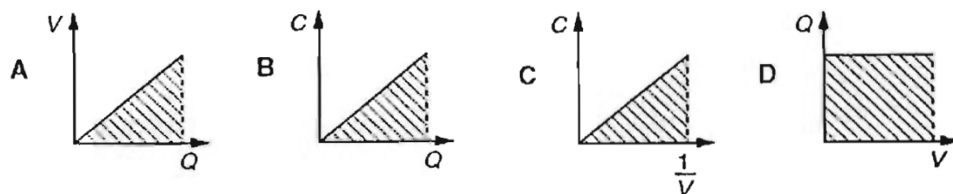- 1.5** The energy stored in a capacitor of capacitance C , carrying charge Q with potential difference V between its plates, may be obtained by calculating the area under an appropriate graph.

Which graph shows the correct relationship between a pair of the quantities C , Q and V , and in addition shows a shaded area which corresponds to the energy stored in the capacitor?



Answer: A

$C = Q / V$ and energy stored in capacitor $= \frac{1}{2} QV = \frac{1}{2} CV^2 = \frac{1}{2} \frac{Q^2}{C}$. So

Option A: Graph of V against Q gives a straight line with gradient $= 1/C$.

Area under graph $= \frac{1}{2} QV = \text{energy stored}$

Option B: Graph of C against Q gives a straight line with gradient $= 1/V$.

Area under graph $= \frac{1}{2} QC \neq \text{energy stored}$


Option C: Graph of C against $1/V$ gives a straight line with gradient $= Q$.

Area under graph $= \frac{1}{2} C \left(\frac{1}{V} \right) = \frac{1}{2} \frac{C}{V} \neq \text{energy stored}$

Option D: Graph of Q against V cannot be a horizontal line.

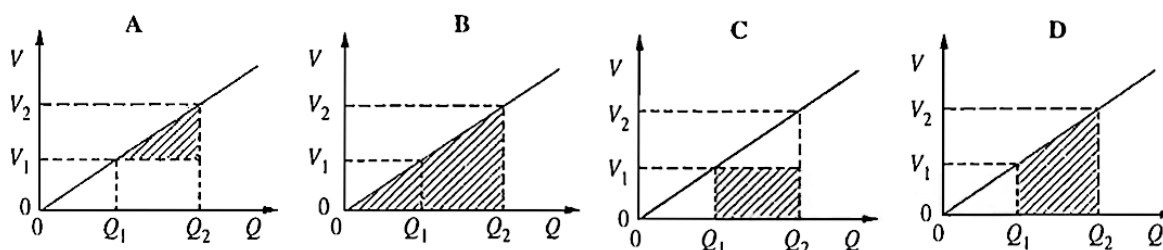- 1.6** When the potential difference V between the plates of a capacitor is increased from V_1 to V_2 , the charge Q on the plates increases from Q_1 to Q_2 .

On the graphs, which shaded area represents the increase in the energy stored in the capacitor?




Answer: D

Initial energy stored $= \frac{1}{2} Q_1 V_1$

Final energy stored $= \frac{1}{2} Q_2 V_2$

Increase in energy stored $= \frac{1}{2} Q_2 V_2 - \frac{1}{2} Q_1 V_1$

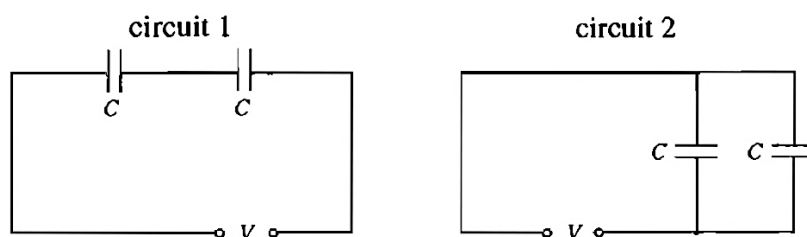- 1.7** The diagrams show two ways of connecting two identical capacitors of capacitance C in circuits each with a supply of p.d. V .



What is the value of $\frac{\text{total energy stored in the capacitors in circuit 1}}{\text{total energy stored in the capacitors in circuit 2}}$?

- A** 0.25 **B** 0.50 **C** 2.0 **D** 4.0

Answer: A

Circuit 1: Equivalent capacitor $C_{\text{total}} = (1/C + 1/C)^{-1} = C/2$
 p.d. across equivalent capacitor = V
 Energy stored = $\frac{1}{2} (C/2) V^2 = \frac{1}{4} CV^2$

Circuit 2: Equivalent capacitor $C_{\text{total}} = C + C = 2C$
 p.d. across equivalent capacitor = V
 Energy stored = $\frac{1}{2} (2C) V^2 = CV^2$

Ratio = $\frac{1}{4} / 1 = 0.25$

- 1.8** A capacitor is charged to a voltage V and then discharged through a small d.c. motor. As the capacitor discharges, the motor raises a mass through a height h . The experiment is repeated for several values of V .

A constant fraction of the capacitor energy is converted to gain of gravitational potential energy.

Which graph would be expected to give a straight line?

- A** h against V^2 **B** h against V
C h against $\sqrt{V}$ **D** h against $1/\sqrt{V}$

Answer: A

Energy stored in capacitor $U = \frac{1}{2} CV^2$


Energy transferred to gravitational potential store = $k \times U = mgh$ where k is a constant < 1 .

$$k \times \frac{1}{2} CV^2 = mgh$$

$$h = \frac{kC}{2mg} V^2$$

Since k , C , m and g are constant, a graph of h against V^2 will give a straight line.

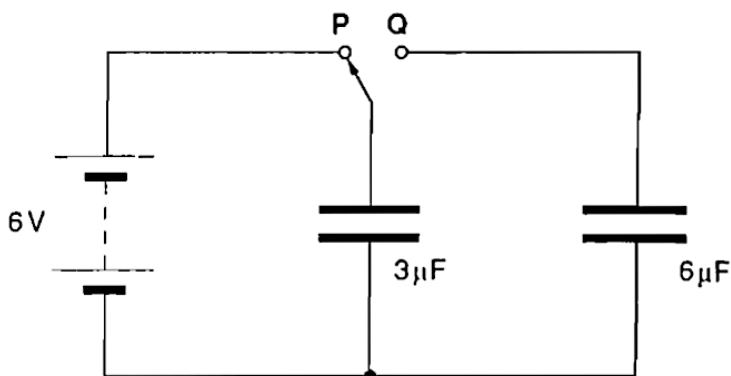- 1.9** In the circuit shown, a capacitor of capacitance $3\ \mu\text{F}$ is charged from a battery of e.m.f. $6\ \text{V}$ with the switch connected to terminal **P**.



The switch is now connected to **Q**. This charges the $6\ \mu\text{F}$ capacitor from the $3\ \mu\text{F}$ one.

What is the new potential difference across the combination?

- A** 1 V **B** 2 V **C** 4 V **D** 6 V

Answer: B

Before connecting to Q, charge on $3\ \mu\text{F}$ capacitor = $(3)(6) = 18\ \mu\text{C}$

After connecting to Q,

equivalent capacitance of parallel connected capacitors = $3 + 6 = 9\ \mu\text{F}$

charge on equivalent capacitor = $18\ \mu\text{C}$

p.d. across equivalent capacitor $V = Q / C = 18 / 9 = 2\ \text{V}$

- 1.10** A capacitor of capacitance C_1 is charged to a potential difference of $100\ \text{V}$ and then disconnected. When a second uncharged capacitor of capacitance C_2 is connected in parallel across it, the new p.d. is $60\ \text{V}$.

What is the value of the ratio $\frac{C_1}{C_2}$?

- A** 0.60 **B** 0.67 **C** 1.50 **D** 1.67

Answer: C

Before connecting to C_2 capacitor, charge on C_1 capacitor = $100C_1$

After connecting to C_2 capacitor,

equivalent capacitance of parallel connected capacitors = $C_1 + C_2$

charge on equivalent capacitor = $100C_1$

p.d. across equivalent capacitor $V = Q / C = 100C_1 / (C_1 + C_2) = 60\ \text{V}$

$$\frac{C_1 + C_2}{100C_1} = \frac{1}{60}$$

$$1 + \frac{C_2}{C_1} = \frac{100}{60}$$

$$\frac{C_1}{C_2} = \frac{60}{40} = 1.50$$